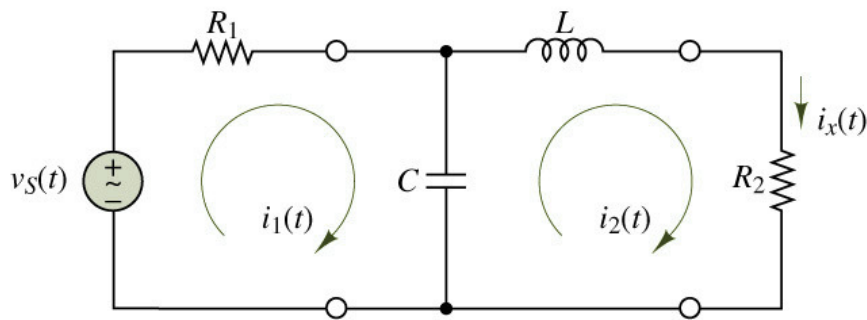



# Class 10 (3/6) AC circuit analysis

- Procedure to solve a problem
  - Identify the sinusoidal and note the excitation frequency.
  - Convert the source(s) to phasor form
  - Represent each circuit element by its impedance
  - Solve the resulting phasor circuit using previous learnt analysis tools
  - Convert the (phasor form) answer to its time domain equivalent.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




A sample circuit  
for AC analysis

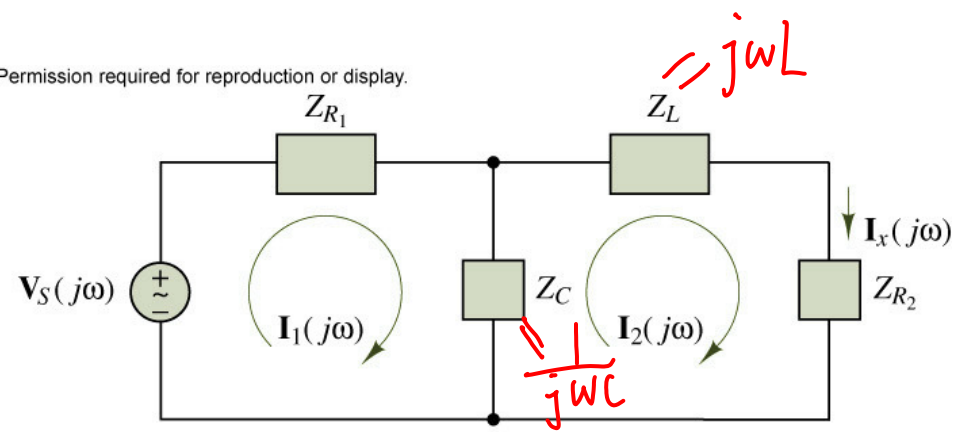

The same circuit  
in phasor form

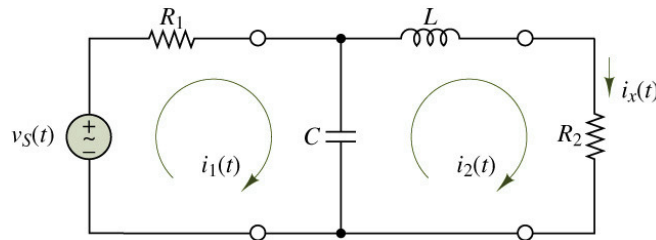
# Ex. 4.21 P200

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



A sample circuit for AC analysis

$= 10^{-6} \text{ F}$

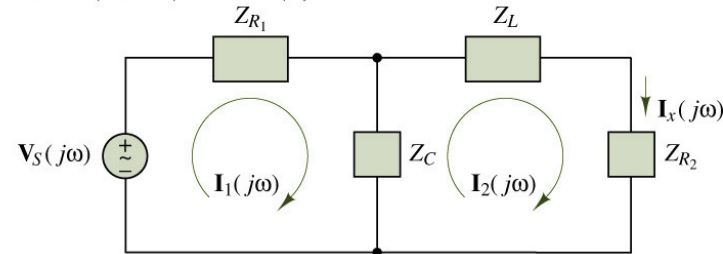

The same circuit in phasor form

$R_1=100 \Omega$ ,  $R_2=75 \Omega$ ,  $C=1 \mu\text{F}$ ,  $L=0.5 \text{ H}$ ,  $v_S(t)=15\cos(1500t) \text{ V}$ .

Determine  $i_1(t)$  and  $i_2(t)$ .

Step 1:  $v_S(t)=15\cos(1500t)$ ,  $\omega=1500 \text{ rad/s}$ .

Step 2:  $V_S(j\omega)=15 \angle 0$

Step 3:  $Z_{R1}=R_1$ ,  $Z_{R2}=R_2$ ,  $Z_C=1/j\omega C$ ,  $Z_L=j\omega L$


Step 4: mesh equation

$$\begin{aligned} (Z_{R1} + Z_C)I_1(j\omega) - Z_C I_2(j\omega) &= V_S(j\omega) \\ -Z_C I_1(j\omega) + (Z_C + Z_L + Z_{R2})I_2(j\omega) &= 0 \end{aligned}$$

In text book, mesh equations are written based on KVL

$$V_S(j\omega) - Z_{R1}I_1(j\omega) - Z_C(I_1(j\omega) - I_2(j\omega)) = 0$$
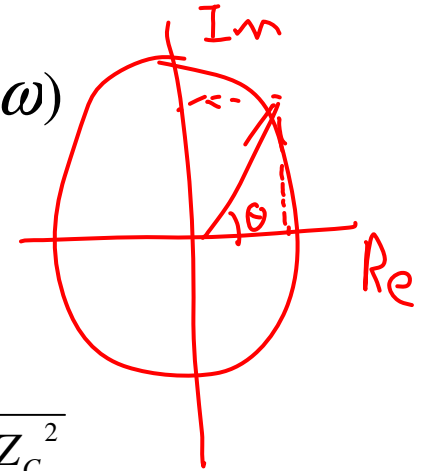
$$\begin{aligned} (Z_{R1} + Z_C)I_1(j\omega) - Z_C I_2(j\omega) &= V_S(j\omega) \\ -Z_C I_1(j\omega) + (Z_C + Z_L + Z_{R2})I_2(j\omega) &= 0 \end{aligned}$$



$$I_1(j\omega) = \frac{\begin{vmatrix} V_S(j\omega) & -Z_C \\ 0 & Z_C + Z_L + Z_{R2} \end{vmatrix}}{\begin{vmatrix} Z_{R1} + Z_C & -Z_C \\ -Z_C & Z_C + Z_L + Z_{R2} \end{vmatrix}} = \frac{(Z_C + Z_L + Z_{R2})V_S(j\omega)}{(Z_{R1} + Z_C)(Z_C + Z_L + Z_{R2}) - Z_C^2}$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j1500 \times 10^{-6}} = \frac{66.7}{j} = -66.7 j \Omega$$

$10^{-6} \text{ F} = C = 1 \mu\text{F}$ ,  $L = 0.5 \text{ H}$ ,  
 $R_1 = 100 \Omega$ ,  $R_2 = 75 \Omega$ ,  
 $v_s(t) = 15 \cos(1500t) \text{ V}$

$$Z_L = j\omega L = j1500 \times 0.5 = 750 j (\Omega)$$

$$I_1(j\omega) = \frac{(75 + 683j)15 \angle 0}{(100 - 66.7j)(75 + 683j) + 4450}$$

$$\sqrt{(57550)^2 + (63300)^2}$$

$$\begin{aligned} 7500 + 45600 - 5000j + 68300j + 4450 &= 57550 + 63300j \\ &= 85500 \angle 47.8 \end{aligned}$$

$$\tan^{-1} \left( \frac{63300}{57550} \right)$$

$$I_1(j\omega) = \frac{687 \angle 83.7 \cdot 15 \angle 0}{85500 \angle 47.8} = 0.012 \angle 35.9^\circ = 0.012 \angle 0.63$$

$$i_1(t) = 0.012 \cos(1500t + 0.63) (\text{A})$$

# Norton & Thevenin

- Norton & Thevenin equivalent circuits are calculated the same way as before except using the phasor.

# Superposition principle

- For multiple sources of the same or different frequencies, final results are the superposition of individual result from single source by setting all other sources to be zero