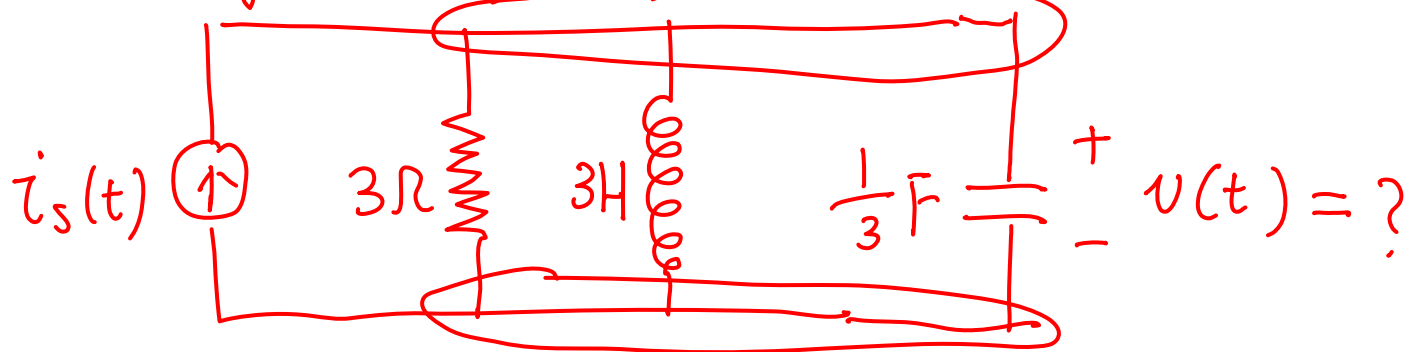


Solve for voltage v in circuit below



$$i_s(t) = 10 \cos 2t \quad (\text{A})$$

$$I_s(j\omega) = 10 \angle 0^\circ$$

$$Z_R = 3\Omega \quad Z_L = j\omega L = j \cdot 2 \cdot 3 = 6j \Omega$$

$$Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -\frac{j}{2 \cdot \frac{1}{3}} = -1.5j \Omega$$

$$Z_{eq} = ?$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L}$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L}}$$

do it yourself !

Slight different approach

$$Z_{eq} = (Z_R // Z_L) // Z_C$$

$$= \frac{Z_R \cdot Z_L}{Z_R + Z_L} // Z_C$$

$$= \frac{3 \times 6j}{3 + 6j} // Z_C$$

$$= \frac{6j(1-2j)}{(1+2j)(1-2j)} // Z_C$$

$$= \frac{12 + 6j}{5} // Z_C$$

$$= (2.4 + 1.2j) // (-1.5j)$$

$$= \frac{(2.4 + 1.2j)(-1.5j)}{2.4 + 1.2j - 1.5j}$$

$$= \frac{(1.8 - 3.6j)(2.4 + 0.3j)}{(2.4 - 0.3j)(2.4 + 0.3j)}$$

$$(1+2j)(1-2j)$$

$$= 1 - (2j)^2$$

$$= 1 - (-4) = 5$$

$$Z_{eq} = \frac{5.4 - 8.1j}{(2.419)^2}$$

$$= (0.923 - 1.385j) \Omega$$

$$\text{modulus} = \sqrt{(0.923)^2 + (1.385)^2} = 1.66$$


$$\text{angle} = \tan^{-1}\left(\frac{-1.385}{0.923}\right) = -56.3^\circ$$

$$Z_{eq} = 1.66 \angle -56.3^\circ$$


$$V(j\omega) = I_s(j\omega) Z_{eq} = (10 \angle 0^\circ) \cdot (1.66 \angle -56.3^\circ)$$

$$V(j\omega) = 16.6 \angle -56.3^\circ$$

$$v(t) = 16.6 \cos(2t - 56.3^\circ)$$

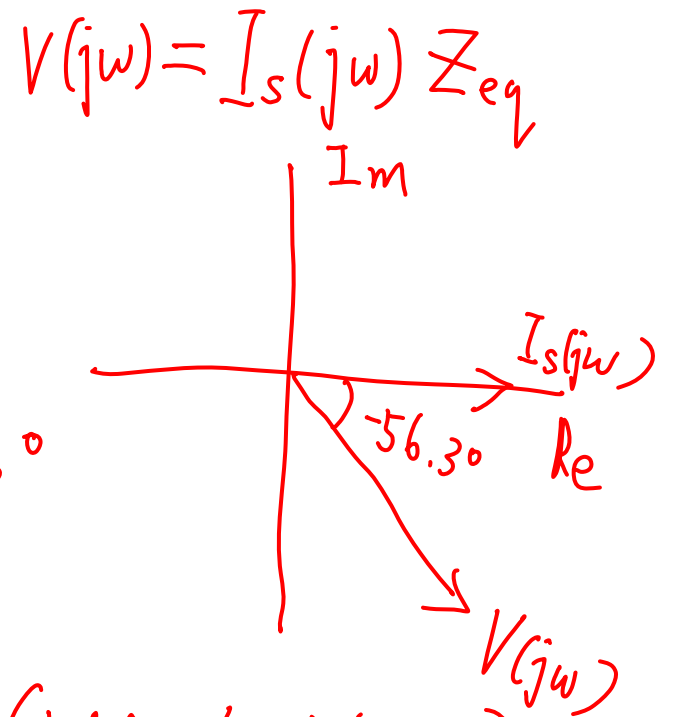

Determine the current in each branch

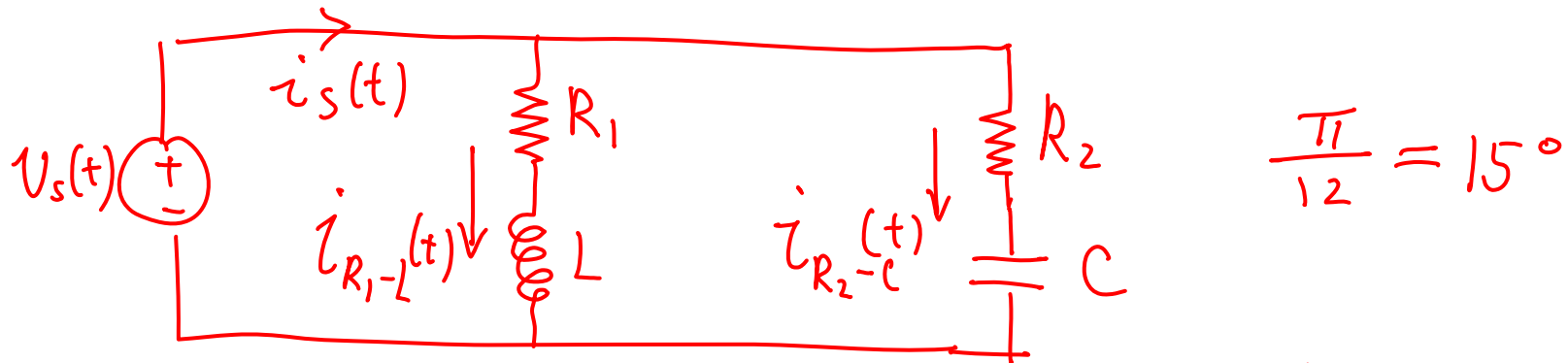

$$v_s(t) = 636 \cos\left(3000t + \frac{\pi}{12}\right) \text{ (V)}$$

$$R_1 = 3.3 \text{ k}\Omega \quad R_2 = 22 \text{ k}\Omega \quad L = 1.90 \text{ H} \quad C = 6.8 \text{ nF}$$

$$i_s(t) = ?$$

$$V_s(j\omega) = 636 \angle 15^\circ$$

$$Z_{R_1} = 3300 \Omega \quad Z_{R_2} = 22000 \Omega$$

$$Z_L = j\omega L = j(3000 \times 1.9) = 5700j \Omega$$

$$Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -\frac{j}{3000 \times (6.8 \times 10^{-9})} = -4.9 \times 10^4 j \Omega$$

$$Z_{eq} = (Z_C + Z_{R2}) // (Z_L + Z_{R1})$$

$$= \frac{(Z_C + Z_{R2})(Z_L + Z_{R1})}{Z_C + Z_{R2} + Z_L + Z_{R1}}$$

$$= \frac{(22000 - 4.9 \times 10^4 j)(5700 j + 3300)}{22000 + 3300 - 4.9 \times 10^4 j + 5700 j}$$

$$= \frac{(22000 - 49000 j)(3300 + 5700 j)}{25300 - 43300 j}$$

$$= \frac{(53712 \angle -65.8^\circ) \cdot (6586 \angle 59.9^\circ)}{50149 \angle -59.7^\circ}$$

$$= 7054 \angle 53.8^\circ \quad \Omega$$

$$I_s(j\omega) = \frac{V_s(j\omega)}{Z_{eq}} = \frac{636 \angle 15^\circ}{7054 \angle 53.8^\circ} = 0.090 \angle -38.8^\circ$$

$$i_s(t) = 0.090 \cos(3000t - 38.8^\circ) \quad (A)$$

$$i_{R_1-L} = ? \quad I_{R_1-L}(j\omega)$$

$$I_{R_1-L}(j\omega) = \frac{V_s(j\omega)}{Z_L + Z_{R_1}} = \frac{636 \angle 15^\circ}{6586 \angle 59.9^\circ}$$
$$= 0.096 \angle -44.9^\circ$$


$$i_{R_1-L}(t) = 0.096 \cos(3000t - 45^\circ)$$

$$i_{R_2-C}(t) = ?$$

$$I_{R_2-C}(j\omega) = \frac{V_s(j\omega)}{Z_C + Z_{R_2}} = \frac{636 \angle 15^\circ}{53712 \angle -65.8^\circ}$$
$$= 0.012 \angle 80.8^\circ$$

$$i_{R_2-C}(t) = 0.012 \cos(3000t + 80.8^\circ)$$

Mesh analysis

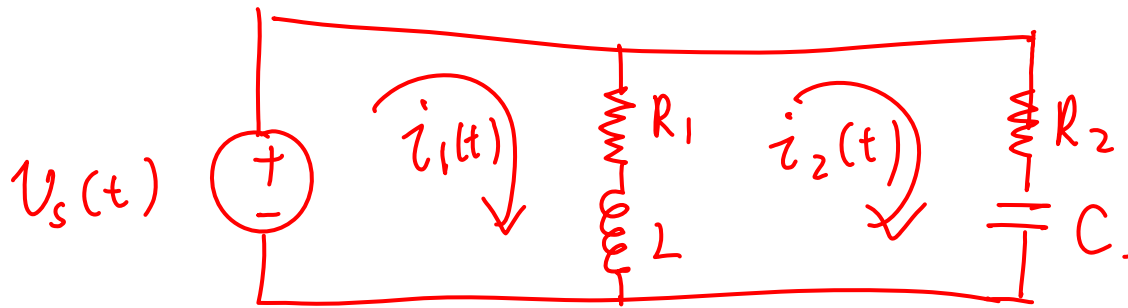

$$V_s(j\omega) = 636 \angle 15^\circ$$

$$I_1(j\omega) = ? \quad I_2(j\omega) = ?$$

$$(Z_{R_1} + Z_L) I_1(j\omega) - (Z_{R_1} + Z_L) I_2(j\omega) = V_s(j\omega)$$

$$-(Z_{R_1} + Z_L) I_1(j\omega) + (Z_{R_1} + Z_L + Z_{R_2} + Z_C) I_2(j\omega) = 0$$

$$I_1(j\omega) = \frac{\begin{vmatrix} V_s(j\omega) & -(Z_{R_1} + Z_L) \\ 0 & (Z_{R_1} + Z_L + Z_{R_2} + Z_C) \end{vmatrix}}{\begin{vmatrix} Z_{R_1} + Z_L & -(Z_{R_1} + Z_L) \\ -(Z_{R_1} + Z_L) & (Z_{R_1} + Z_L + Z_{R_2} + Z_C) \end{vmatrix}}$$

$$\begin{aligned}
I_1(j\omega) &= \frac{V_s(j\omega)(Z_{R_1} + Z_L + Z_{R_2} + Z_C)}{(Z_{R_1} + Z_L + Z_{R_2} + Z_C)(Z_{R_1} + Z_L) - (Z_{R_1} + Z_L)^2} \\
&= \frac{V_s(j\omega)(Z_{R_1} + Z_L + Z_{R_2} + Z_C)}{(Z_{R_2} + Z_C)(Z_{R_1} + Z_L)} \\
&= \frac{(636 \angle 15^\circ)(50149 \angle -59.7^\circ)}{(53712 \angle -65.8^\circ)(6586 \angle 59.9^\circ)} \\
&= 0.090 \angle -38.8^\circ
\end{aligned}$$

$$i_1(t) = 0.090 \cos(300t - 38.8^\circ)$$