

Kirchhoff's voltage law (KVL): Cont.

The sum of voltages around a closed loop is zero.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

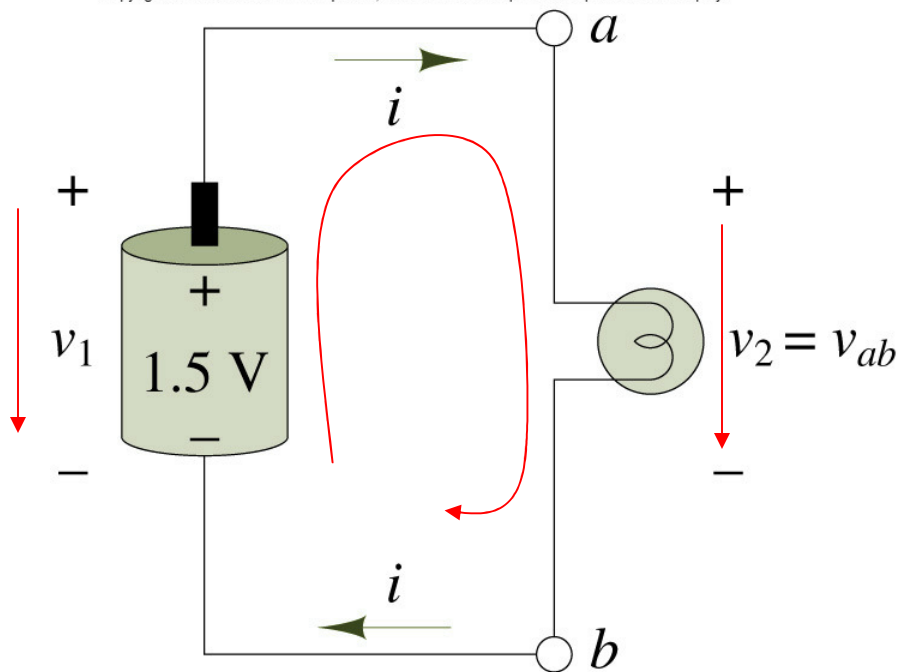


Illustration of Kirchhoff's voltage law: $v_1 = v_2$

$$-V_1 + V_2 = 0$$

Voltage difference (V) vs. Voltage (V)


Voltage: at each node, v_a, v_b
Voltage difference: $v_2 = v_a - v_b$

Ground (point of zero voltage):


- true ground (earth)
- chassis ground (enclosure)

Class 2 (2/15F) Circuit Elements and Their i - v Characteristics


Resistance and Ohm's Law:

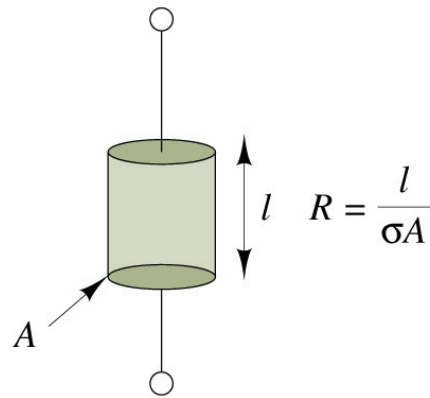

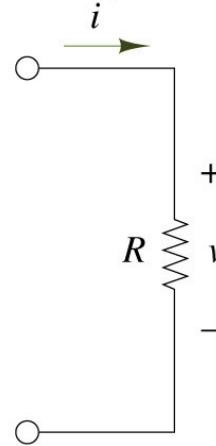Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Circuit symbol

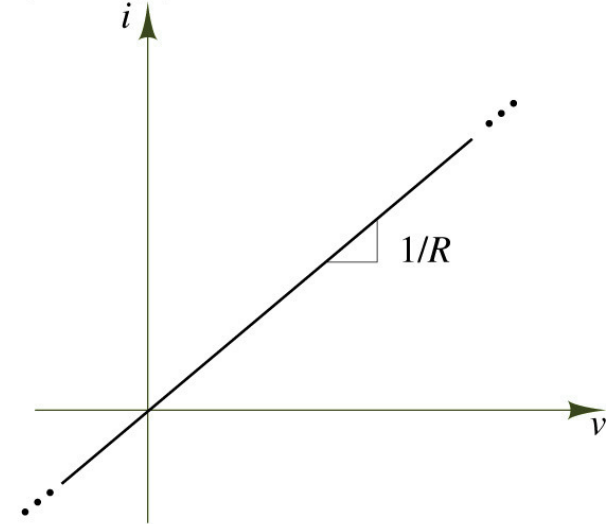

i - v characteristic


$$R = \frac{V}{I}$$

Physical resistors with resistance R . Typical materials are carbon, metal film.

$$R = \rho \frac{L}{A} = \# \Omega \cdot \text{m} \times \frac{\text{m}}{\text{m}^2} = \# \Omega$$

$$\sigma = \frac{1}{\rho}$$

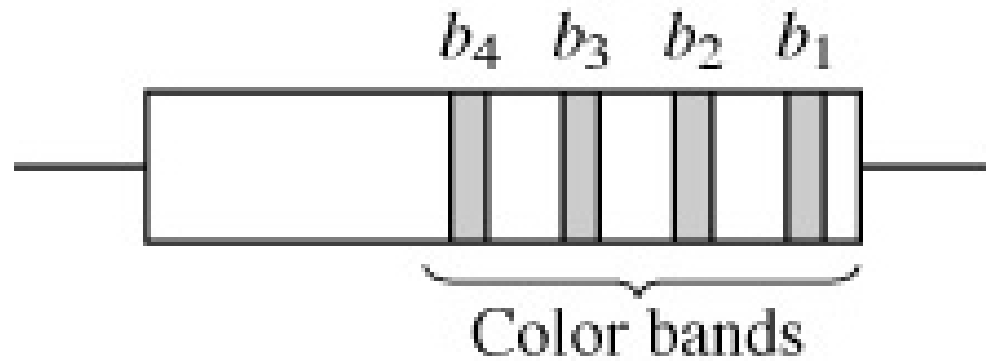Resistance (R) depends on materials and geometry, and resistivity (ρ) only depends on materials.



black	0	blue	6
brown	1	violet	7
red	2	gray	8
orange	3	white	9
yellow	4	silver	10%
green	5	gold	5%

Resistor value = $(b_1 b_2) \times 10^{b_3}$;
 $b_4 = \% \text{ tolerance in actual value}$

Table 2.3 Resistance of copper wire

AWG size	Number of strands	Diameter per strand (in)	Resistance per 1,000 ft (Ω)
24	Solid	0.0201	28.4
24	7	0.0080	28.4
22	Solid	0.0254	18.0
22	7	0.0100	19.0
20	Solid	0.0320	11.3
20	7	0.0126	11.9
18	Solid	0.0403	7.2
18	7	0.0159	7.5
16	Solid	0.0508	4.5
16	19	0.0113	4.7
14	Solid	0.0641	2.52
12	Solid	0.0808	1.62
10	Solid	0.1019	1.02
8	Solid	0.1285	0.64
6	Solid	0.1620	0.4
4	Solid	0.2043	0.25
2	Solid	0.2576	0.16

Electric Power

Electric power: moving charge → doing work (energy)

$$\text{Power (P)} = \text{Work} / \text{time} = \text{work} / \text{charge} \times \text{charge} / \text{time} = V I$$

$$P = \text{Joules} / \text{sec} = \text{Watts (W)}$$

What are we paying for electricity bill ?

$$\text{kW H} = \text{energy}$$

More on Resistance

Home electric appliances: what does a 1000 W hair dryer tell you?

- Always assume 120V if the voltage is not specified.

$$P = iV \Rightarrow i = \frac{P}{V} = \frac{1000}{120} = 8.33 \text{ (A)}$$

$$P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{120^2}{1000} = 14.4 \text{ (\Omega)}$$

- **Never exceed the rated power.**
- Can you use these appliances in 220 V lines.


$$P = \frac{V^2}{R} = \frac{220^2}{14.4} = 3661 \text{ (W)}$$

You destroy the appliance!


You can use appliances rated with 220V in 110 V, but with much lower power than rated. (Exercise)

Open and Short Circuits

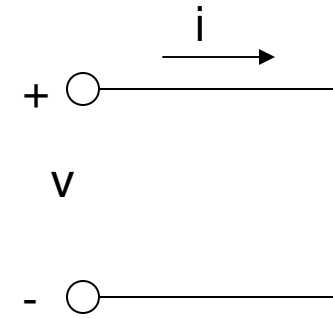- Short Circuit: $R=0$, $v=0$ for any i .
 - Particularly bad for voltage source.



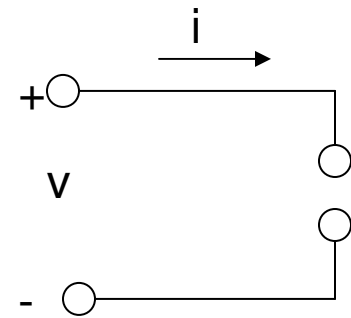- Open Circuit: $R \rightarrow \infty$, $i=0$ for any v .
 - Particularly bad for current source.



Series Resistors and the Voltage Divider

Rule

- Series Circuit: One branch → same current through each resistor.

$$1.5V = v_1 + v_2 + v_3$$

$$= i_1 R_1 + i_2 R_2 + i_3 R_3$$

$$= i(R_1 + R_2 + R_3)$$

$$i_1 = i_2 = i_3 = i$$

$$1.5V = iR_{EQ}$$

$$R_{EQ} = R_1 + R_2 + R_3$$

In general for N resistors in series :

$$R_{EQ} = \sum_{n=1}^N R_n, \quad i = i_1 = \dots = i_N, \quad v = \sum_{n=1}^N v_n$$


For a series resistors : $R_{EQ} > (R_1, R_2, \dots, R_N)$

Voltage Divider:

$$v_1 = \frac{R_1}{R_{EQ}} (1.5V)$$


$$v_2 = \frac{R_2}{R_{EQ}} (1.5V)$$

$$v_3 = \frac{R_3}{R_{EQ}} (1.5V)$$

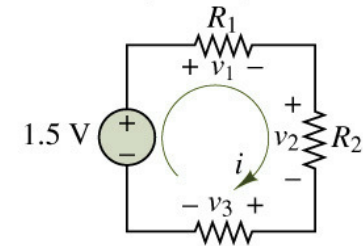

The current i flows through each of the four series elements. Thus, by KVL,

$$1.5 = v_1 + v_2 + v_3$$

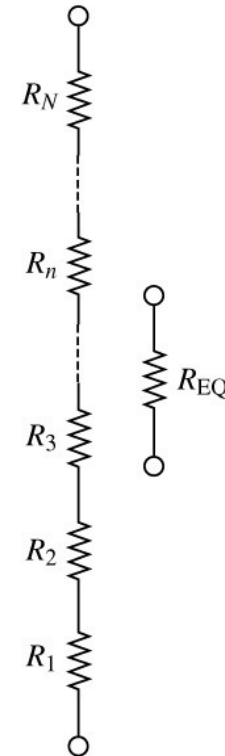

N series resistors are equivalent to a single resistor equal to the sum of the individual resistances.