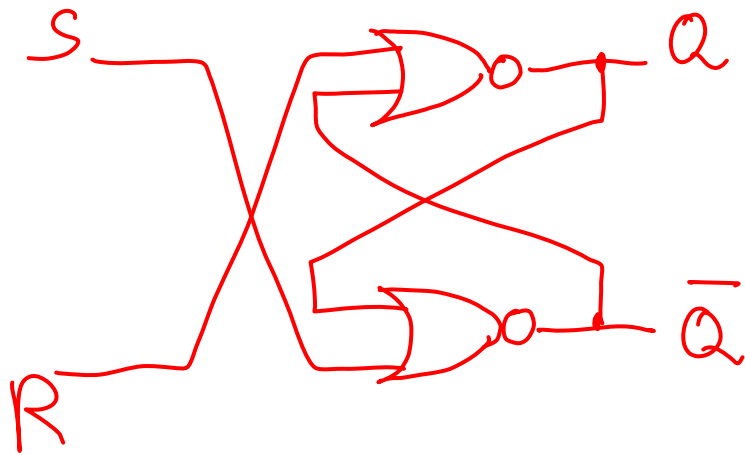


# Inside of RS FF's


NOR gate RS latch



S	R	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
0	0	1	0
0	0	0	1

→ unstable


With Enable

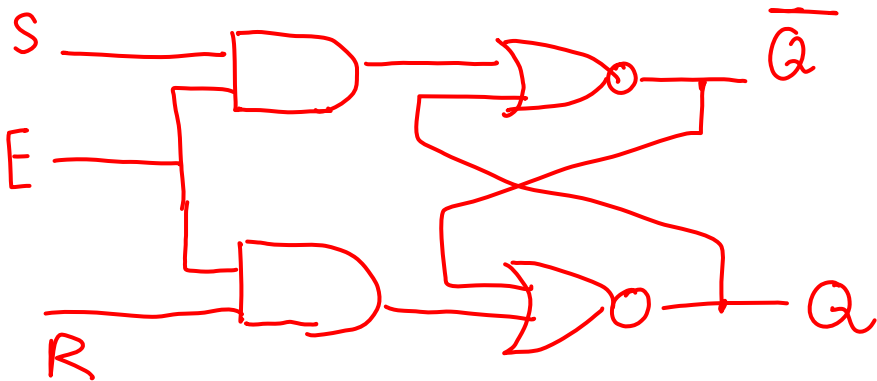

0	0	1	0	} two possibilities
		0	1	
1	1	undetermined		
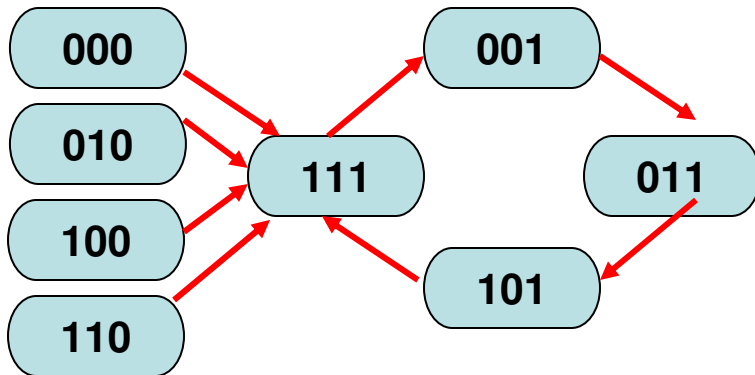
# Sequential Logic Design

- **State Diagram (State transition table):** A Case Study: design an 3-bit counter that only counts 1,3,5,7 using D FF
- How many outputs do we need? 3 (encode the states)




Truth Table

Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>
0	0	1	0	1	1
0	1	1	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1
0	0	0	1	1	1
0	1	0	1	1	1
1	0	0	1	1	1
1	1	0	1	1	1

- For unused states, usually reset to 000, or 111, or if not particularly required, can be labeled as d (don't care) (or x)
- Construct the truth table: write down current state (Q<sub>1</sub>Q<sub>2</sub>Q<sub>3</sub>•••) and use current state to prepare the inputs of FF's to go into the next state specified in the state diagram.
  - Outputs of FF's (Q<sub>1</sub>Q<sub>2</sub>Q<sub>3</sub>•••) are inputs in the truth table, inputs of FF's (D<sub>1</sub>D<sub>2</sub>D<sub>3</sub>•••) are outputs in the truth table.
- Use Karnaugh map to design the circuit

# Sequential Logic Design

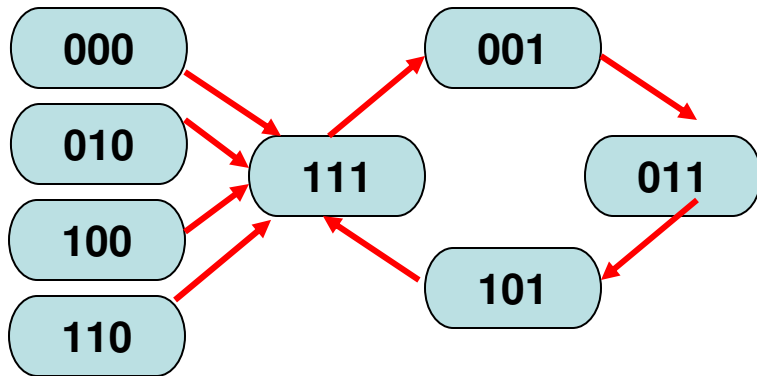

Red supercell:  $Q_1'$   
 Green supercell:  $Q_2'$

**Draw circuit**


**Truth Table**

$Q_3$	$Q_2$	$Q_1$	$D_3$	$D_2$	$D_1$
0	0	1	0	1	1
0	1	1	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1
0	0	0	1	1	1
0	1	0	1	1	1
1	0	0	1	1	1
1	1	0	1	1	1

The Karnaugh map for  $D_2$  is:

	$Q_1$	0	1
$Q_3Q_2$			
00		1	1
01		1	0
11		1	0
10		1	1

# Sequential Logic Design

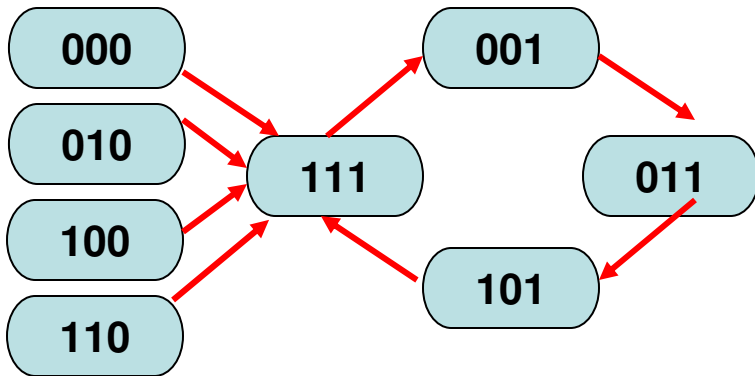

Red supercell:  $Q_1'$   
 Green supercell:  $Q_2Q_3'$   
 Gray supercell:  $Q_2'Q_3$   
 $D_1: Q_1' + Q_2Q_3' + Q_2'Q_3$   
 $D_2: Q_1' + Q_2'$   
 $D_3: 1$

Draw circuit with CLK.

Real Applications:

- odd number generator
- B-game score counter: CLK is input

Truth Table

$Q_3$	$Q_2$	$Q_1$	$D_3$	$D_2$	$D_1$
0	0	1	0	1	1
0	1	1	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1
0	0	0	1	1	1
0	1	0	1	1	1
1	0	0	1	1	1
1	1	0	1	1	1

The Karnaugh map for  $D_3$  is:

	$Q_1$	0	1
$Q_3Q_2$			
00		1	0
01		1	1
11		1	0
10		1	1

$$D_1: \bar{Q}_1 + Q_2 \bar{Q}_3 + \bar{Q}_2 \cdot Q_3$$

$$D_2: \bar{Q}_1 + \bar{Q}_2$$

$$D_3: 1$$

