

In capacitor

$V_c(t)$ is continuous

$$i = \frac{dq}{dt} = C \frac{dV_c(t)}{dt} \neq \infty$$


at $t < 0$

$$V_c = 95V$$

at $t=0^+$

$$i = \frac{(130 - 95)V}{(23 + 7)k\Omega} = \frac{35V}{30k\Omega} = 1.17mA$$

$$Z_c = \frac{1}{j\omega C}$$

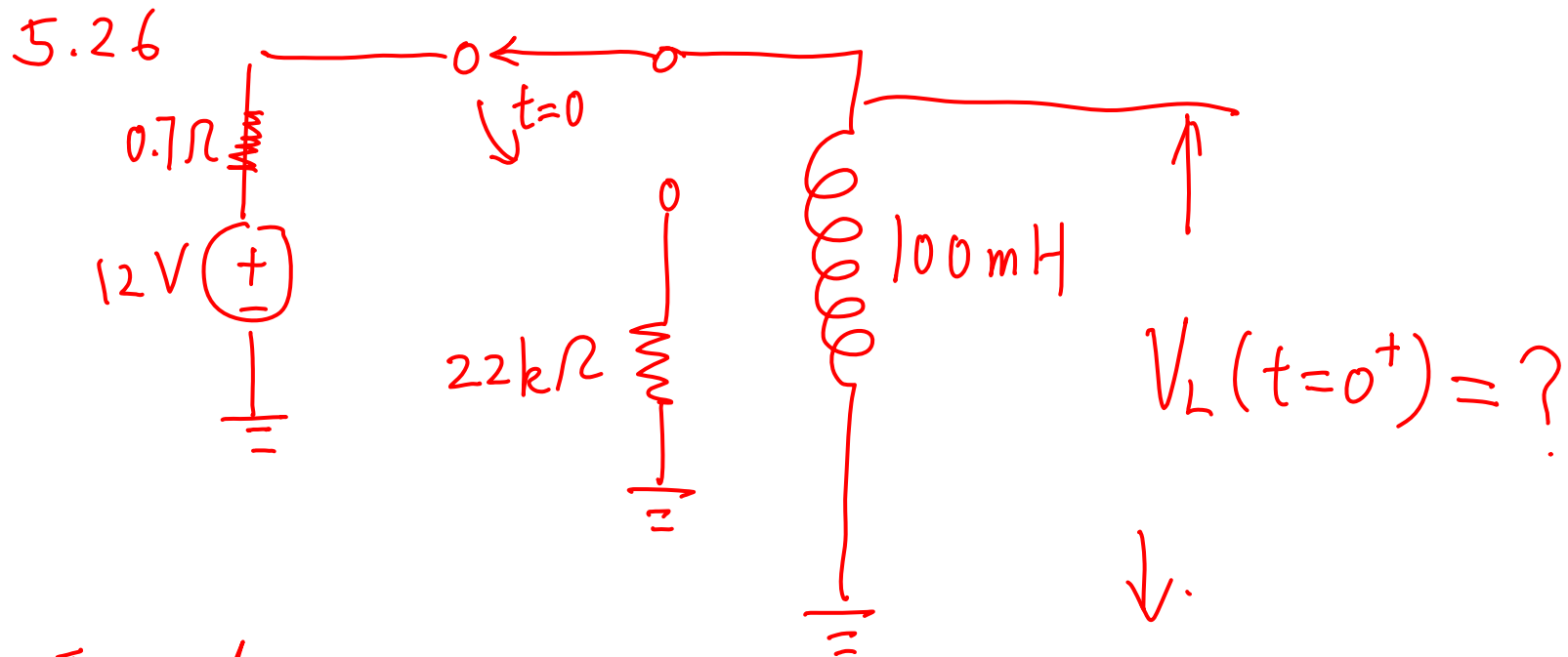

In inductor $i(t)$ is continuous

$$V_L = L \frac{di(t)}{dt} = \infty$$


at $t < 0$

$$i_L = \frac{12V}{0.7\Omega} = 17.1(A)$$

at $t = 0^+$

$$V_L = -V_R = -i_L \cdot 22k\Omega = -(17.1A) \cdot (22k\Omega) \\ = 376 (kV)$$

5.34

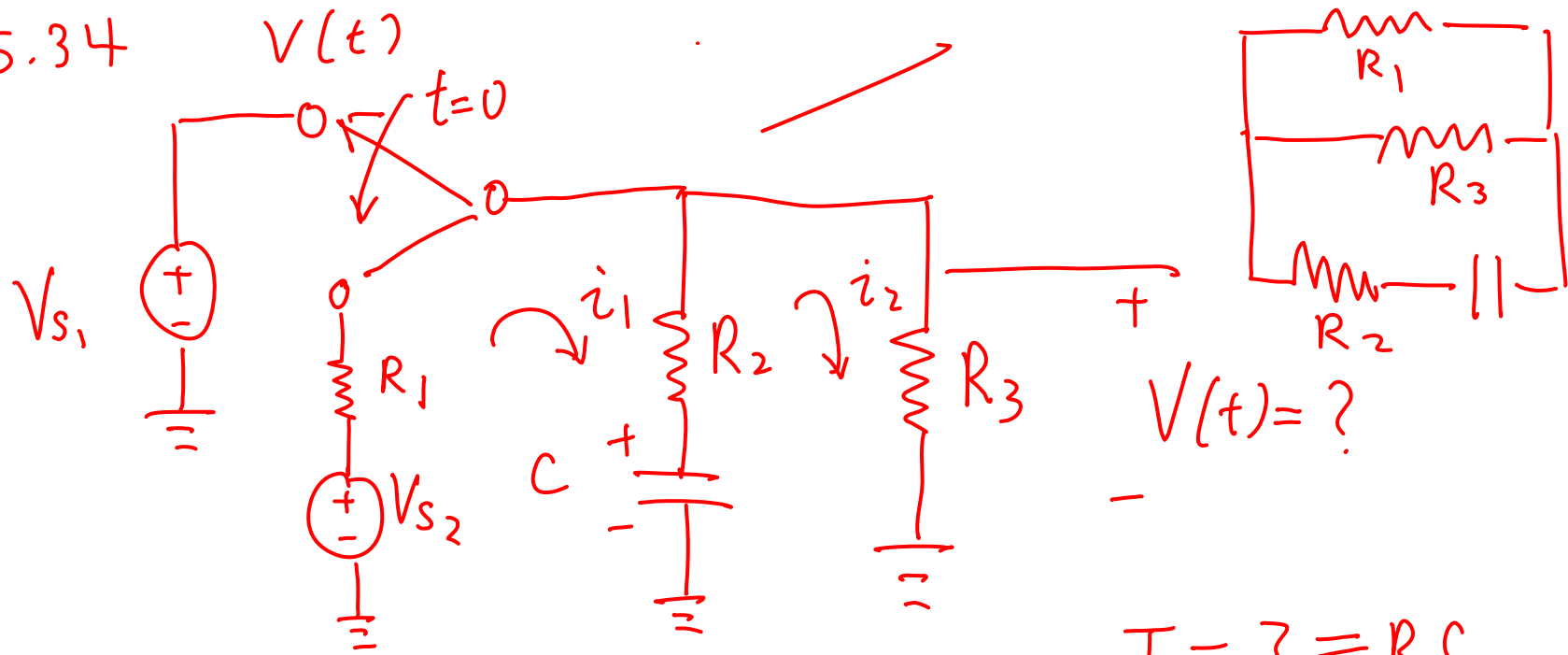

At $t < 0$ $V_C = V_{S_1} = 17V$

$V_{R_3} = 17V$

$t = 0^+$ $i_1(0^+)$ $i_2(0^+)$

$V(0^+) = i_2(0^+) R_3$

$t = \infty$ $V(\infty) = R_3 \frac{V_{S_2}}{R_1 + R_3}$

$V(t) = V(\infty) + (V(0^+) - V(\infty)) e^{-\frac{t}{\tau}}$

$V(t) = ?$

$\tau = ? = R_{eq} C$

$= (R_1 // R_3 + R_2) C$

$= \left(\frac{R_1 R_3}{R_1 + R_3} + R_2 \right) C$