
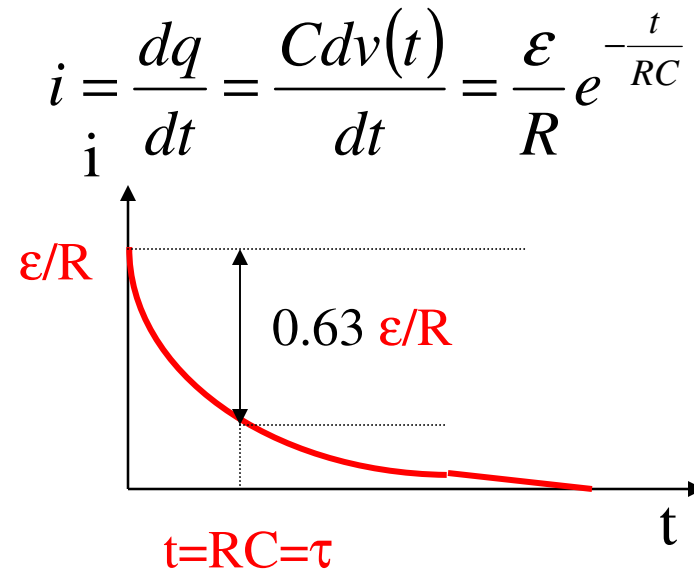


## Charging a Capacitor

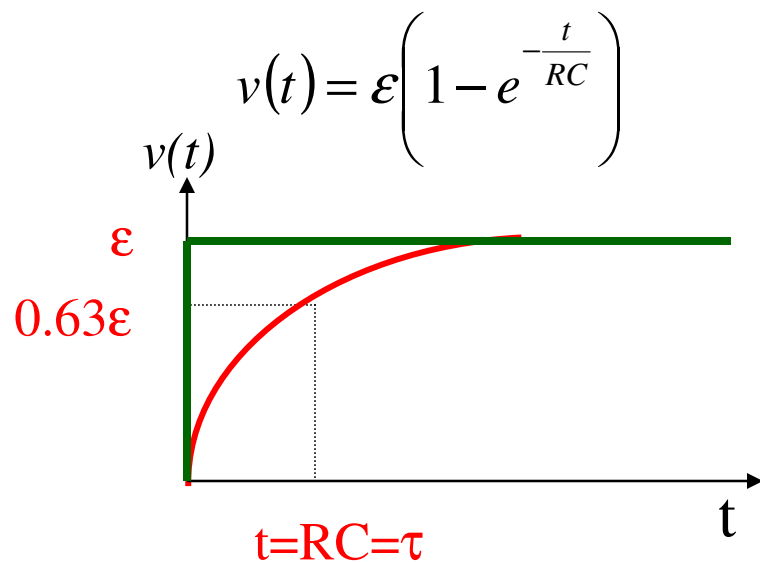



Time constant ( $\tau$ ): time needs to charge a capacitor to 63% of its full charge.

The larger the  $RC$ , the longer it takes to charge a capacitor.

The larger the  $R$  value, the smaller the current is in the circuit.


The larger the  $C$  value, the more the charge the capacitor can hold

## Discharging a Capacitor

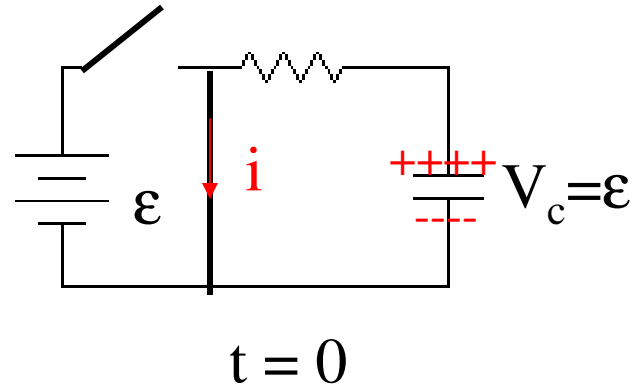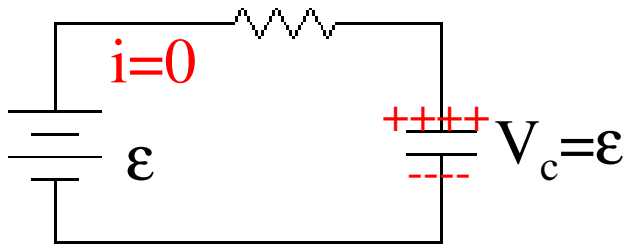


$$v(t) = \mathcal{E} e^{-\frac{t}{RC}}$$
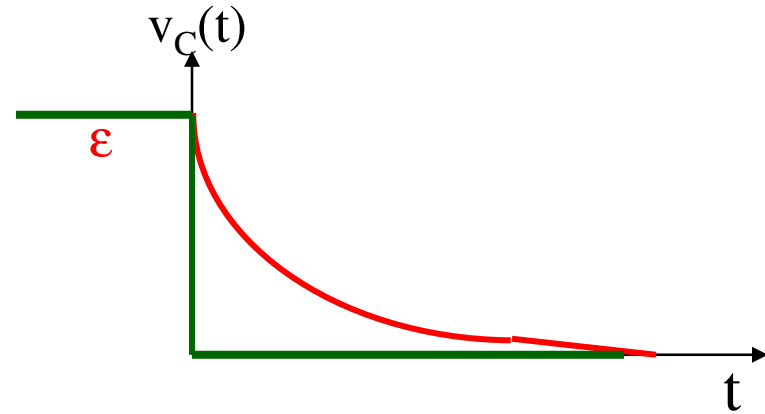
$$i = \left( \frac{\mathcal{E}}{R} \right) e^{-\frac{t}{RC}}$$




## Example

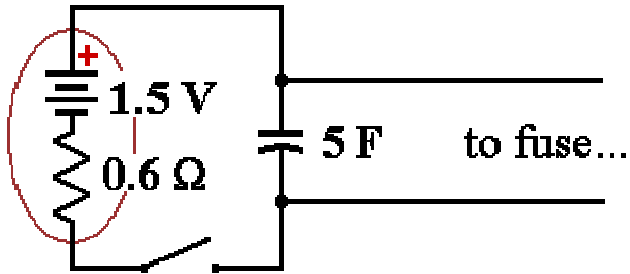a) A young MacGyver enthusiast is attempting to design a simple switched RC circuit to use as a fuse timer. The child has a 5 F capacitor and one AAA cell with an emf of 1.5 V and an internal resistance of 0.6 ohm. If the fuse will ignite when the capacitor is charged to a voltage of 1.0 V, how much time does the youngster have to vacate the premises?




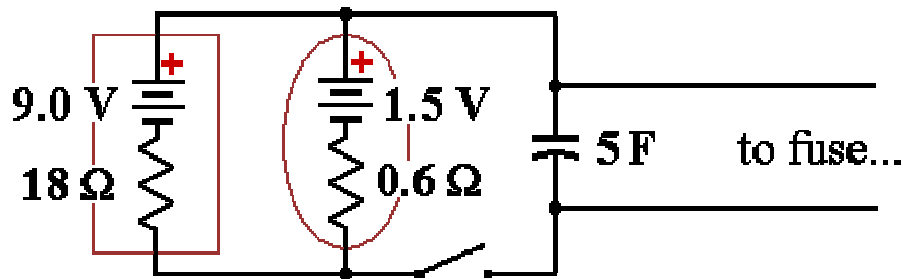b). With a never ending enthusiasm for adding batteries to a circuit, the youngster connects a fresh 9 V lithium battery as shown. Now how much time expires after switch closure until the fuse is ignited?



## Example

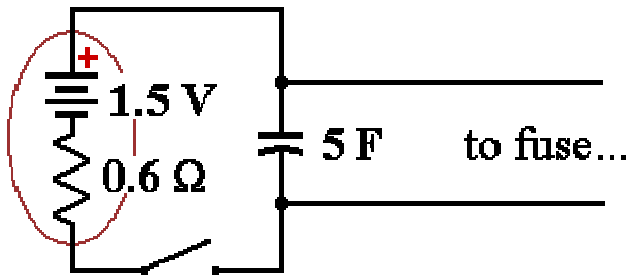a) A young MacGyver enthusiast is attempting to design a simple switched RC circuit to use as a fuse timer. The child has a 5 F capacitor and one AAA cell with an emf of 1.5 V and an internal resistance of 0.6 ohm. If the fuse will ignite when the capacitor is charged to a voltage of 1.0 V, how much time does the youngster have to vacate the premises?




$$V_C = V_S \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$t = -RC \ln \left( 1 - \frac{V_C}{V_S} \right)$$

$$= -0.6 \times 5 \ln \left( 1 - \frac{1.0}{1.5} \right)$$


$$= 3.3 \text{ sec}$$

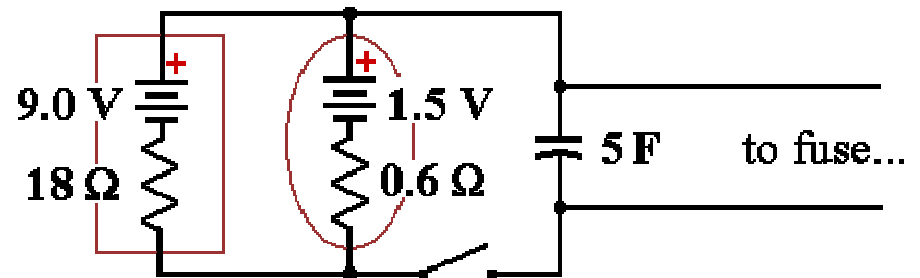b). With a never ending enthusiasm for adding batteries to a circuit, the youngster connects a fresh 9 V lithium battery as shown. Now how much time expires after switch closure until the fuse is ignited?



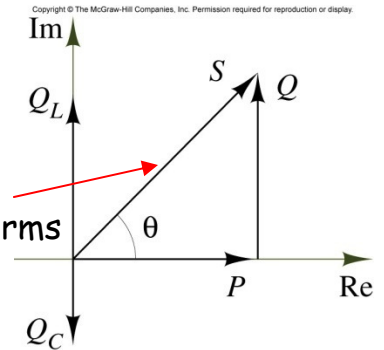
# Chapter 7: Complex Power Recap

- Why do we use  $S = \widetilde{VI}^*$  <sup>rms!</sup>  $= P_{av} + jQ$ 
  - It a fictitious power for simplification
  - But its absolute value can be measured



Note:  $S = P_R + jQ_C + jQ_L$

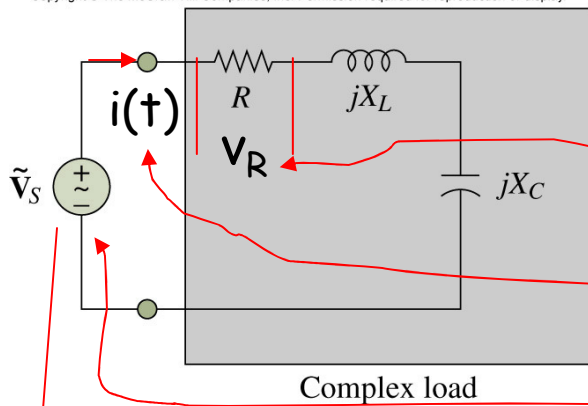Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Calculation of  $P_{av}$ : power dissipated on R (heating the toast, dry your hair, washing your cloth...useful work!)


Method 1:  $P_{av} = (I_R)_{rms} (V_R)_{rms}$ ,  $(I_R)_{rms} = (V_R)_{rms} / R$

Method 2:  $P_{av} = (I_R)_{rms} (V_S)_{rms} \cos\theta$

$$v_s(t) = V_p \cos(\omega t) = V_p \angle 0$$

$$i(t) = I_p \cos(\omega t - \theta) = I_p \angle -\theta$$

$$I_p = \frac{V_p}{|Z|}$$

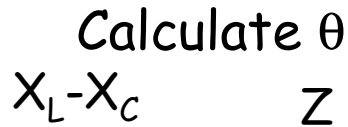

$$I_{rms} = \frac{I_p}{\sqrt{2}}$$


$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

Calculation of Q: total power stored in L and C, not used, exchanged between L & C and source. Would like to minimize so no extra power requirement on the source.

Method 1:  $Q_L = (I_L)_{rms} (V_L)_{rms}$ ,  $(I_L)_{rms} = (V_L)_{rms} / \omega L$   
 $Q_C = (I_C)_{rms} (V_C)_{rms}$ ,  $(I_C)_{rms} = (V_C)_{rms} \omega C$

Method 2:  $Q = Q_L + Q_C = (I)_{rms} (V_S)_{rms} \sin\theta$


## Review cont.: Complex Power

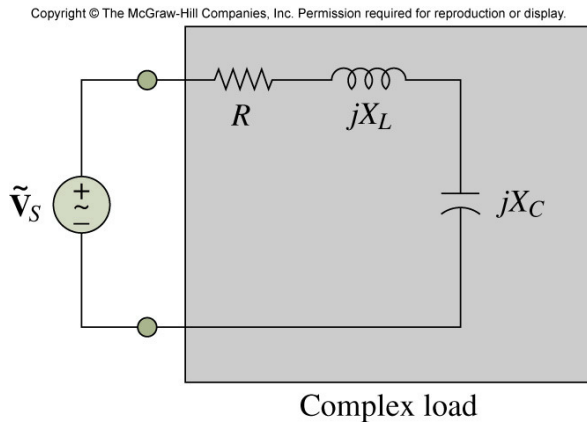

Instantaneous power  $p(t)$

$$S = \tilde{V}\tilde{I}^* = \tilde{I}^2 Z^* = \tilde{V}^2 / Z^*$$

$$= P_{av} + jQ$$

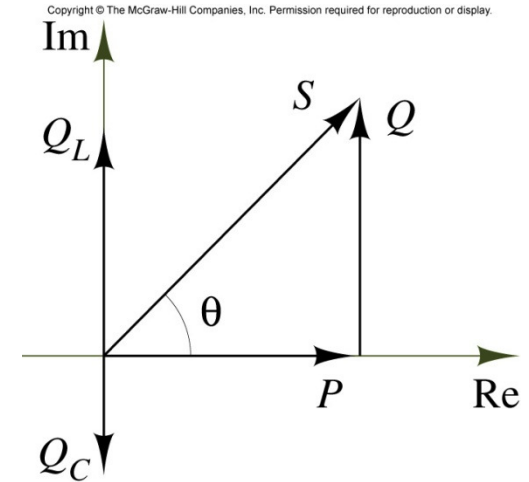

**Pay attention to complex conjugate** Note:  $S = P_R + jQ_C + jQ_L$

- real power  $P_{av}$ : power absorbed by the load resistance.
- $Q$  (volt-amperes reactive, VAR): exchange of energy between the source and the reactive part of the load. **No net power is gained or lost during the process.**
- $|S|$ : compute by measuring the rms load voltage and currents without regard for the phase angle.
- if  $Q < 0$ , the load is capacitive,  $Q > 0$ , the load is inductive