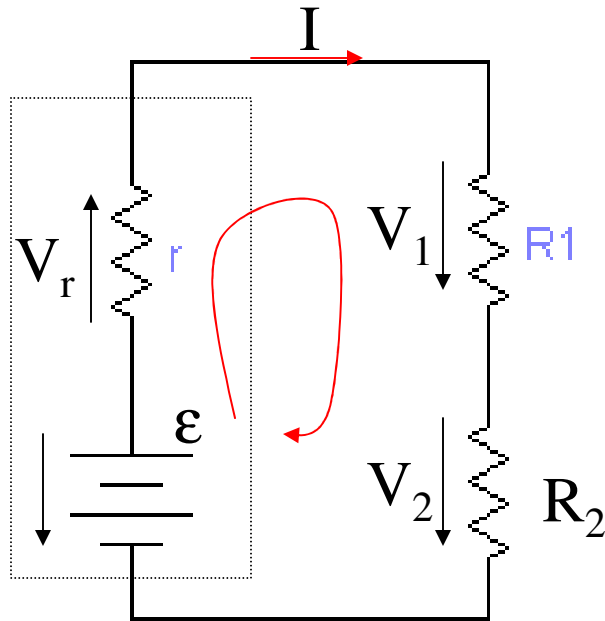


## Method 2a: KVL & KCL

### Kirchhoff's Voltage Law (KVL)

The algebraic sum of voltages around a closed **loop** must be zero




$$-\epsilon + V_r + V_1 + V_2 = 0$$

$$\begin{aligned}\epsilon &= V_r + V_1 + V_2 \\ &= I(r + R_1 + R_2)\end{aligned}$$

$$I = \epsilon / (r + R_1 + R_2)$$

1. For each branch, draw current direction (**arbitrary**) and label the voltage direction (**determined by the current direction**). Voltage on a voltage source is always from positive to negative end.
2. Define either **clockwise** or counterclockwise direction as positive loop direction. **Once the direction is defined, you have to use the same convention in every loop.** The sign for the voltage across each component is positive if voltage direction is the same as the defined loop direction, negative otherwise. (can use current direction to determine the sign)
3. Apply KVL:  $+V$  if  $V$  is in the same direction defined above.

# Kirchhoff's Voltage Law: multiloop

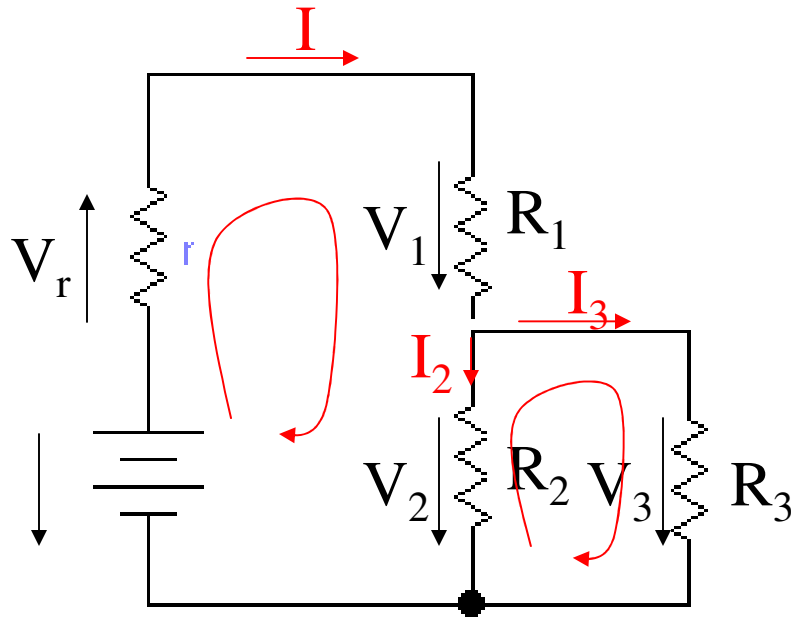


$$-\epsilon + V_r + V_1 + V_2 = 0$$
$$-V_2 + V_3 = 0$$

$$\epsilon = Ir + IR_1 + I_2 R_2$$
$$-I_2 R_2 + I_3 R_3 = 0$$
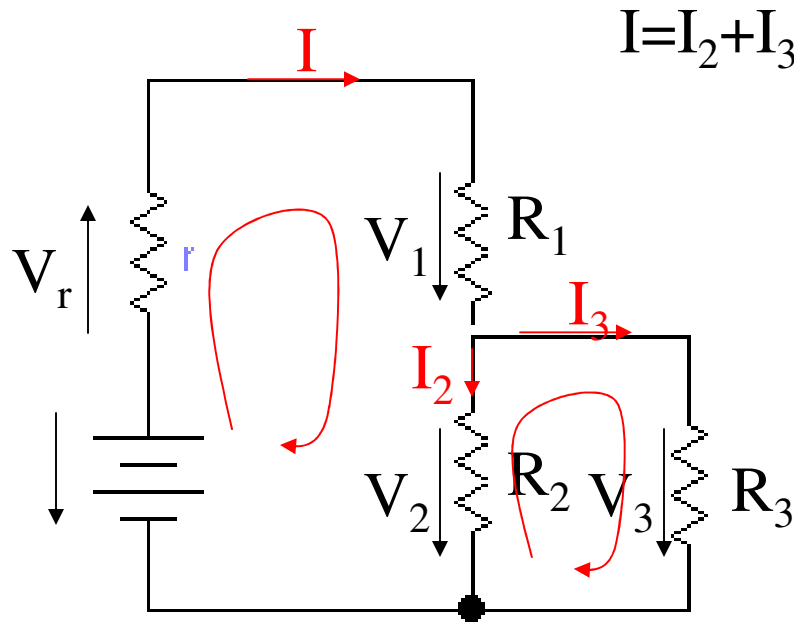
# Kirchhoff's Current Law (KCL)

The algebraic sum of current at a **node** must be zero:  $I_{in} = I_{out}$



$$I = I_2 + I_3 \quad (1)$$

$$\varepsilon = Ir + IR_1 + I_2 R_2 \quad (2)$$

$$-I_2 R_2 + I_3 R_3 = 0 \quad (3)$$

$$\varepsilon = 3 \text{ V}, r = 1 \text{ } \Omega, R_1 = 3 \text{ } \Omega,$$

$$R_2 = 5 \text{ } \Omega, R_3 = 10 \text{ } \Omega$$

$$I - I_2 - I_3 = 0 \quad (4)$$

$$4I + 5I_2 - 0I_3 = 3 \quad (5)$$

$$0I - 5I_2 + 10I_3 = 0 \quad (6)$$

$$\begin{pmatrix} 1 & -1 & -1 \\ 4 & 5 & 0 \\ 0 & -5 & 10 \end{pmatrix} \begin{pmatrix} I \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 3 \\ 0 \end{pmatrix}$$

$$I = \frac{\begin{vmatrix} 0 & -1 & -1 \\ 3 & 5 & 0 \\ 0 & -5 & 10 \end{vmatrix}}{\begin{vmatrix} 1 & -1 & -1 \\ 4 & 5 & 0 \\ 0 & -5 & 10 \end{vmatrix}} = \frac{15 + 30}{50 + 20 + 40} = 0.41 \quad I_2 = \frac{\begin{vmatrix} 1 & 0 & -1 \\ 4 & 3 & 0 \\ 0 & 0 & 10 \end{vmatrix}}{\begin{vmatrix} 1 & -1 & -1 \\ 4 & 5 & 0 \\ 0 & -5 & 10 \end{vmatrix}} = \frac{30 - 0}{50 + 20 + 40} = 0.27$$

Cramer's Rule: Append. A  
 ~~$0(5 \times 10 - (-5) \times 0) - (-1)(3 \times 10 - 0 \times 0) + (-1)(3 \times (-5) - 0 \times 5)$~~


## Last note on KVL & KCL

- If solutions to currents or voltages are negative, they mean the real directions are opposite to what you have defined!
- Deal with current source: current is known, but assign a voltage across the source that has to be solved
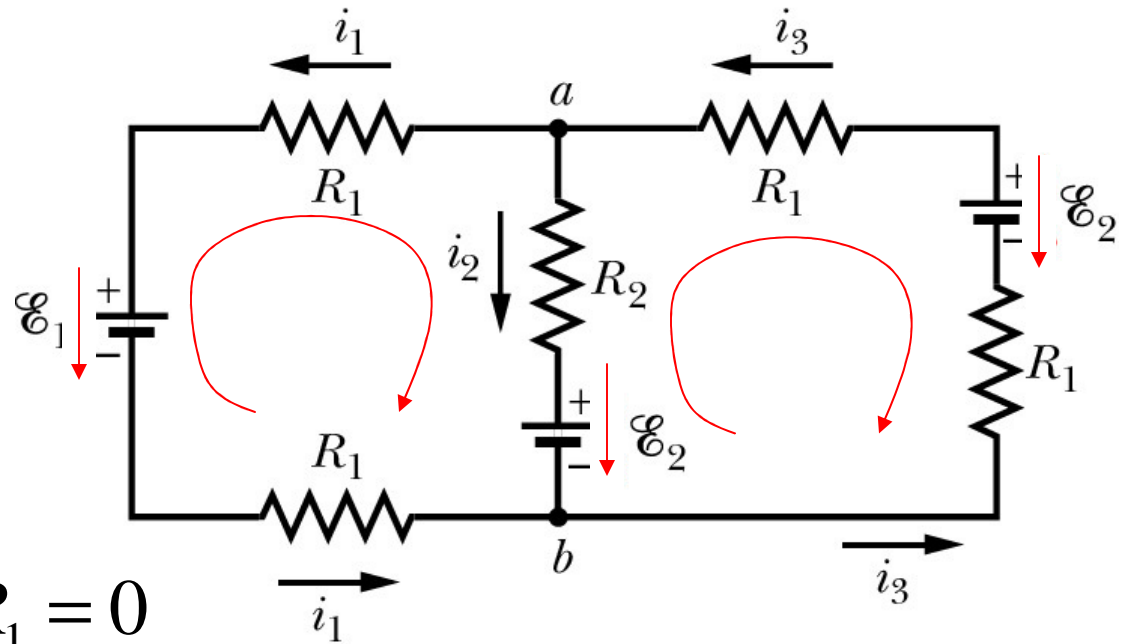
# Sample Problem

Find magnitude and direction of currents

$$\begin{aligned} \mathcal{E}_1 &= 3.0V, & \mathcal{E}_2 &= 6.0V \\ R_1 &= 2.0\Omega, & R_2 &= 4.0\Omega \end{aligned}$$



$$-\mathcal{E}_1 - i_1 R_1 + i_2 R_2 + \mathcal{E}_2 - i_1 R_1 = 0$$

$$-\mathcal{E}_2 - i_2 R_2 - i_3 R_1 + \mathcal{E}_2 - i_3 R_1 = 0$$

$$i_1 + i_2 = i_3$$

$$4i_1 - 4i_2 + 0i_3 = 3$$

$$0i_1 + 4i_2 + 4i_3 = 0$$

$$i_1 + i_2 - i_3 = 0$$

$$i_1 = \frac{\begin{vmatrix} 3 & -4 & 0 \\ 0 & 4 & 4 \\ 0 & 1 & -1 \end{vmatrix}}{\begin{vmatrix} 4 & -4 & 0 \\ 0 & 4 & 4 \\ 1 & 1 & -1 \end{vmatrix}} = \frac{-12 - 12}{-16 - 16 - 16} = 0.5(A)$$

## Method 2b: Mesh analysis

Example: 2 meshes


Step 1: Assignment of mesh currents (clockwise) (mesh is a loop that does not contain other loop).

Step 2: Apply KVL to each mesh

- The so-called self-resistance is the effective resistance of the resistors in series within a mesh. The mutual resistance is the resistance that the mesh has in common with the neighboring mesh.
- To write the mesh equation in standard form, evaluate the self-resistance, then multiply by the mesh current. This will have units of voltage.
- From that, subtract the product of the mutual resistance and the current from the neighboring mesh for each such neighbor.
- Equate the result above to the driving voltage, taken to be positive if its polarity tends to push current in the same direction as the assigned mesh current.

$$\begin{array}{l}
 \text{Mesh 1} \quad (R_1 + R_2)I_1 - R_2I_2 = \varepsilon_1 - \varepsilon_2 \\
 \text{Mesh 2} \quad -R_2I_1 + (R_2 + R_3)I_2 = \varepsilon_2 - \varepsilon_3
 \end{array}$$

Step 3: Solve currents

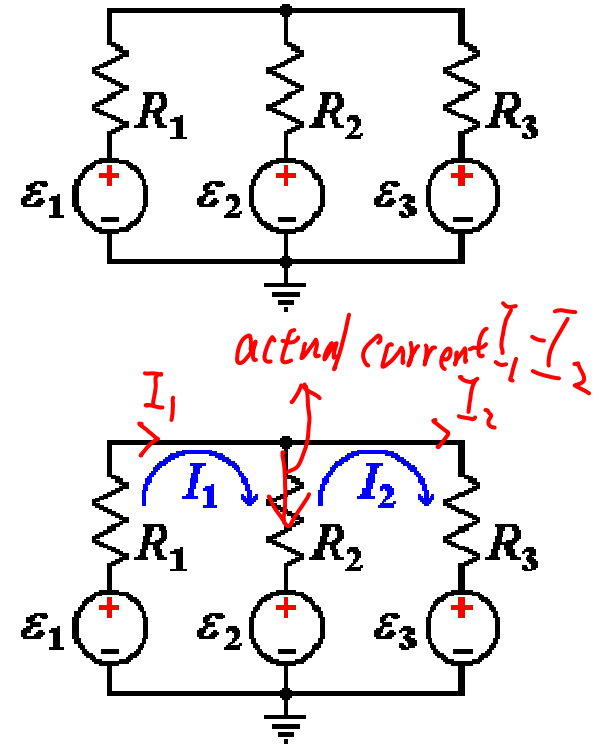

$$\begin{array}{l}
 R_2(I_1 - I_2) \\
 I_1 = I_2 + (I_1 - I_2) \\
 I_1 = I_1
 \end{array}$$

*KCL is implicit*