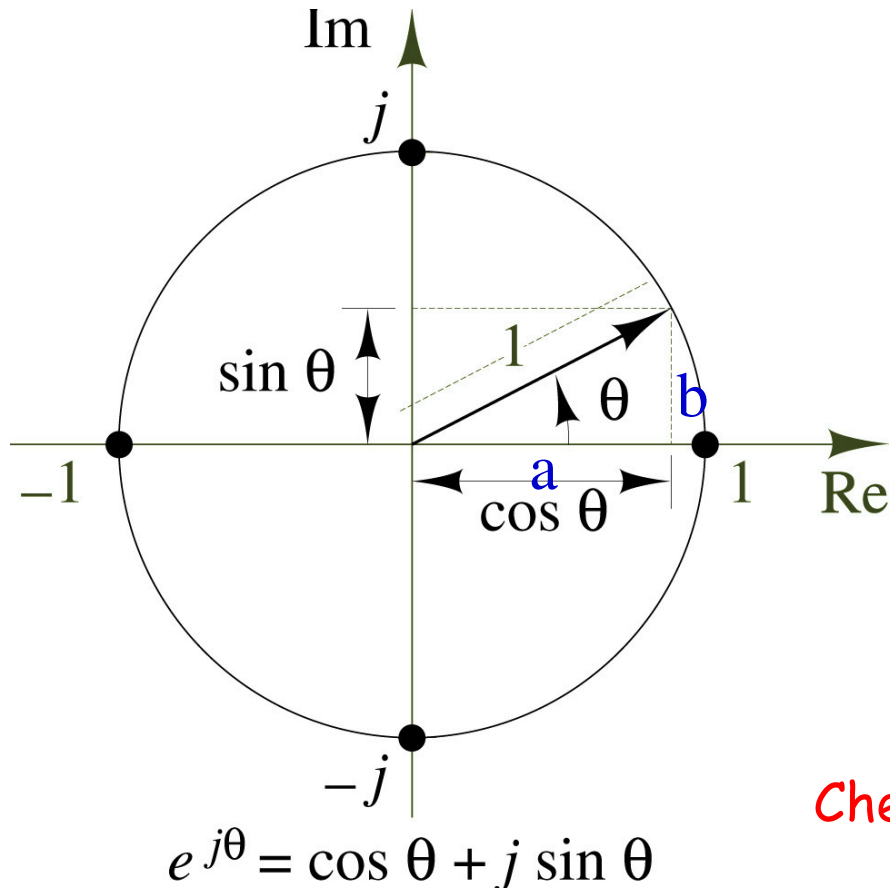


# Complex number review

AC signal  $x(t) = A \cos(\omega t + \phi)$

- freq. does not change in linear circuit
- need compute amplitude  $A$  and phase  $\phi \rightarrow$  need math representation that deal with both quantities  $\rightarrow$  complex number

Euler's identity



$$a + jb = \sqrt{a^2 + b^2} \left( \frac{a}{\sqrt{a^2 + b^2}} + j \frac{b}{\sqrt{a^2 + b^2}} \right)$$

$$= A(\cos \theta + j \sin \theta)$$

$$= Ae^{j\theta}$$

$$= A \angle \theta \quad \mathbf{A: \text{amplitude}, \theta: \text{phase}}$$


$$c_1 = A_1 e^{j\theta_1} = A_1 \angle \theta_1, c_2 = A_2 e^{j\theta_2} = A_2 \angle \theta_2$$

$$c_1 \times c_2 = A_1 A_2 e^{j(\theta_1 + \theta_2)} = A_1 A_2 \angle (\theta_1 + \theta_2)$$

$$\frac{c_1}{c_2} = \frac{A_1}{A_2} e^{j(\theta_1 - \theta_2)} = \frac{A_1}{A_2} \angle (\theta_1 - \theta_2)$$

Check Appendix A for complex number help

# Phasor Animation

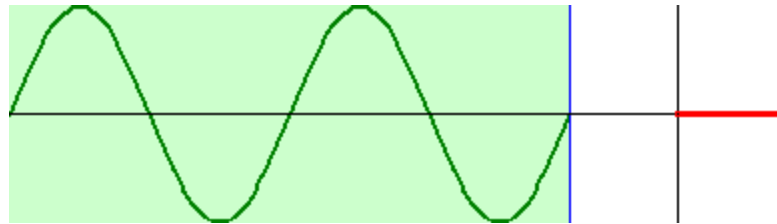

sinPlotting1.swf

# Phasor

How can an ac quantity be represented by a complex number?

$$A\cos(\omega t + \theta) = \text{Re}[A\cos(\omega t + \theta) + jA\sin(\omega t + \theta)] = \text{Re}(Ae^{j(\omega t + \theta)}) = \text{Re}(Ae^{j\omega t}e^{j\theta})$$

Wait, if you only take real part, why do I need imaginary part. This is only way I can compute the phase,  $\theta$ , conveniently.

Since  $\text{Re}$  and  $e^{j\omega t}$  always exist, for simplicity

$$A\cos(\omega t + \theta) \rightarrow Ae^{j\theta} = A\angle\theta \rightarrow \text{Phasor representation (amplitude \& Phase)}$$


*phasor is a complex number in polar form used to assist the calculation in ac circuits*

In text book, bold uppercase quantity indicate phasor voltage or currents

Note the specific frequency  $\omega$  of the sinusoidal signal, since this is not explicit apparent in the phasor expression

# AC i-V relationship for R, L, and C

Resistive Load

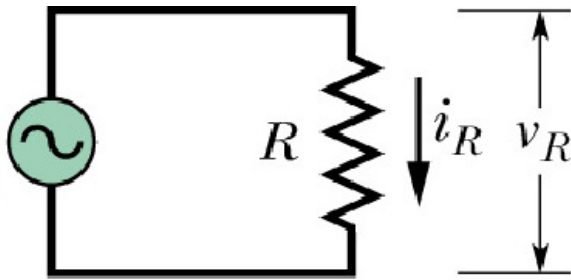


$$\text{Source } v_S(t) = A \sin \omega t$$

$$v_R = v_S(t) = A \sin \omega t$$

$$i_R = \frac{v_R}{R} = \frac{A}{R} \sin \omega t$$

$v_R$  and  $i_R$  are in phase

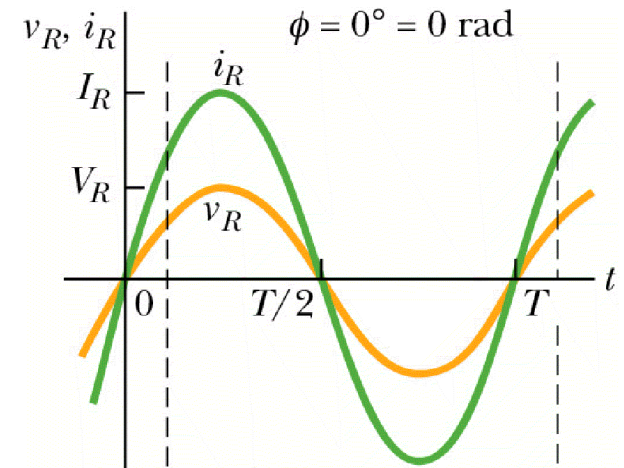

Phasor representation:  $v_S(t) = A \sin \omega t = A \cos(\omega t - 90^\circ) = A \angle -90^\circ = \mathbf{V}_S(j\omega)$



$$\mathbf{I}_S(j\omega) = (A / R) \angle -90^\circ$$

Impedence: complex number of resistance  $Z = \mathbf{V}_S(j\omega) / \mathbf{I}_S(j\omega) = R$

Generalized Ohm's law  $\mathbf{V}_S(j\omega) = Z \mathbf{I}_S(j\omega)$

Everything we learnt before applies for phasors with generalized ohm's law

## Capacitor Load

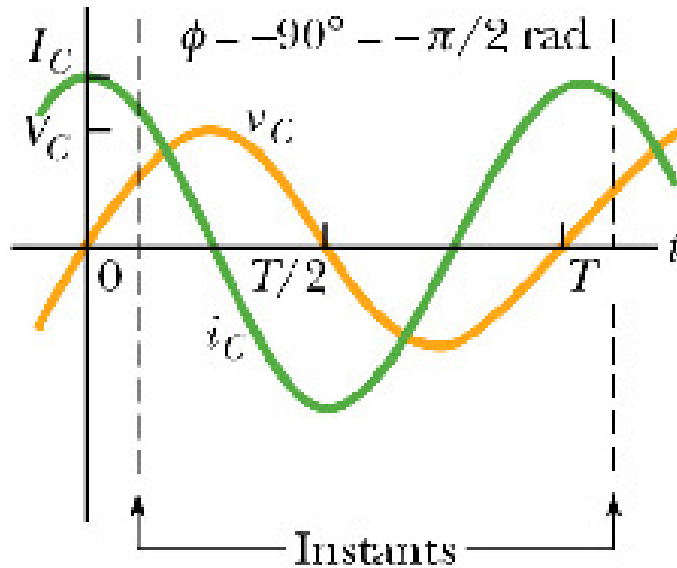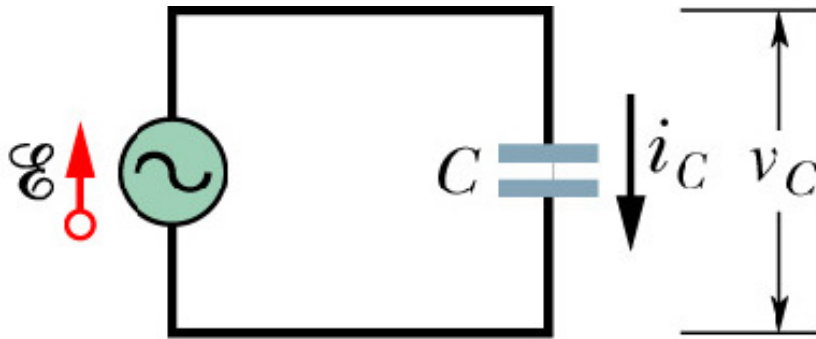

$$v_C = A \sin \omega t$$

$$q_C = C v_C$$

$$i_C = \frac{dq_C}{dt} = \omega C A \cos \omega t$$

$$i_C = \frac{A}{1/\omega C} \sin(\omega t + 90^\circ)$$

ICE

$$\mathbf{V}_C(j\omega) = A \angle -90^\circ$$


$$\mathbf{I}_C(j\omega) = \frac{A}{X_C} \angle 0^\circ$$

$$\mathbf{Z}_C = \frac{\mathbf{V}_C(j\omega)}{\mathbf{I}_C(j\omega)} = X_C \angle -90^\circ$$

$$= \frac{-j}{\omega C} = \frac{-j \cdot j}{j\omega C} = \frac{1}{j\omega C}$$

Notice the impedance of a capacitance decreases with increasing frequency

# Inductive Load

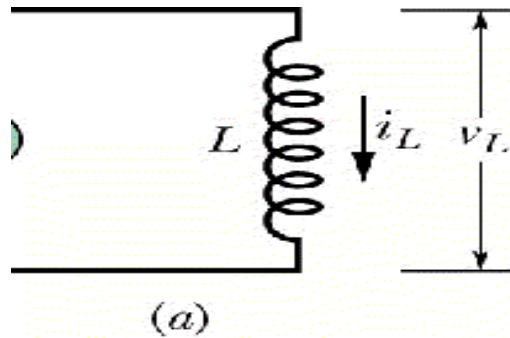


$$v_L = A \sin \omega t$$

$$v_L = L \frac{di_L}{dt}$$

$$i_L = \frac{A}{L} \int \sin \omega t dt = -\left(\frac{A}{\omega L}\right) \cos \omega t$$
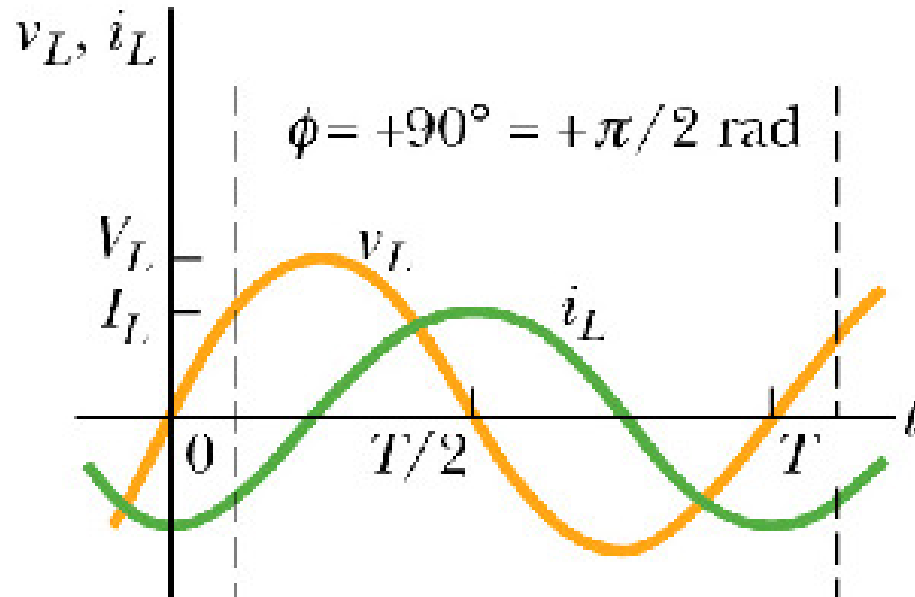
$$i_L = \frac{A}{\omega L} \sin(\omega t - 90^\circ)$$



**ELI**

Phasor:  $\mathbf{V}_L(j\omega) = A \angle -90^\circ$

$\mathbf{I}_L(j\omega) = (A/\omega L) \angle -180^\circ$

$Z_L = j\omega L$

Opposite to  $Z_C$ ,  $Z_L$  increases with frequency

# Impedance

$$Z_R = R \quad Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C} \quad Z_L = j\omega L$$

- Why  $Z_C$  and  $Z_L$  are complex number
  - Since they change the phase of signal. The phase is represented by the imaginary part of the complex number.
- Related questions: What does impedance physically change in a circuit?
  - Real part: amplitude, Imaginary part: phase.